

# CONVERSION OF GALVANOMETER TO VOLTMETER

---

## 1 OBJECTIVES

To convert a galvanometer to voltmeter.

## 2 REQUIREMENTS

Galvanometer, power supply(DC), plug keys, resistance boxes( $0 - 1000\Omega$  and  $0 - 10000\Omega$ )

## 3 INTRODUCTION

A voltmeter is an instrument of high resistance so that when it is connected across an element for measurement, the voltmeter draws a negligible current through it. Suppose we want to convert a galvanometer of resistance  $G$  into a voltmeter of range  $0 - V$  where  $V > I_g G$  where  $I_g$  is the current through the galvanometer. Then the series resistance  $R$  to be connected is given by;

$$\begin{aligned}\frac{V}{R + G} &= I_g \\ \Rightarrow R &= \frac{V}{I_g} - G\end{aligned}\tag{1}$$

## 4 PROCEDURE

### 4.1 To find the resistance $G$ of the galvanometer.

1. Set up the circuit as shown in the circuit diagram.
2. Introduce suitable resistance  $R$  such that with  $K_2$  open and  $K_1$  closed the galvanometer gives a full scale deflection of any  $n$  division.
3. Now introduce some resistance in  $S$  such that the deflection is reduced to half the initial value.
4. Then if  $R$  is very large compared to  $G$ , the resistance introduced in  $S$  is equal to resistance of the galvanometer.

### 4.2 To determine $K$ , the figure of merit of galvanometer.

1. Figure of merit of galvanometer is defined as the current required to produce unit deflection in the galvanometer. Connect the circuit as shown in the diagram.
2. A resistance  $R$  is introduced in the circuit and the deflection  $\theta$  produced in the galvanometer is noted down.
3. The current  $I$  through the galvanometer is given by

$$I = \frac{E}{R + G}$$

where  $E$  is the emf of the cell. The figure of merit of galvanometer is defined by

$$K = \frac{I}{\theta} = \frac{E}{\theta(R + G)} \approx E \times \text{slope}$$

4. The experiment is repeated for various values of R and the mean value of K is noted using a plot of  $\frac{I}{\theta}$  versus R.

#### 4.3 To determine the resistance $R_s$ , required to be added in series

1. If N divisions correspond to full scale deflection of the galvanometer, the current  $I_g$  required to produce full scale deflection is

$$I_g = KN$$

Calculate the value of R to be added to the galvanometer using the relation

$$R = \frac{V}{I_g} - G$$

2. Connect the resistance to the galvanometer in series. Now the galvanometer (V is the range of the voltmeter) can be used as a voltmeter with terminals at A and B. It is used to measure DC voltages in the particular range.

## 5 OBSERVATIONS

### 5.1 Part 1:

Sl. No	R ( $\Omega$ )	S ( $\Omega$ )	G ( $\Omega$ )	Average ( $\Omega$ )

### 5.2 Part 2:

R( $\Omega$ )	$\theta$	$\frac{1}{\theta}$

### 5.3 Part 3:

V(V)	V'(V)	V - V'(V)

## 6 CALCULATIONS

6.1 *Figure of merit of galvanometer.*

$$K = \frac{I}{\theta} = \frac{E}{\theta(R+G)} \approx \frac{E}{R\theta}$$

$E = \text{_____} V$

From the graph,

$$\frac{1}{\theta} = \text{slope} = \text{_____}$$

$$K = E \times \frac{1}{R\theta} = \text{_____}$$

6.2 *To determine the resistance  $R_s$ , required to be added in series*

$$I_g = KN = \text{_____}$$

Value of R to be added to galvanometer

$$R = \frac{V}{I_g} - G = \text{_____}$$

## 7 RESULT

1. The figure of merit of galvanometer, K is \_\_\_\_\_
2. The resistance of the galvanometer is \_\_\_\_\_
3. The resistance in series to be added for conversion into a voltmeter is \_\_\_\_\_

## 8 PRECAUTIONS

Insert a high resistance in the circuit before switching the circuit ON, in order to protect the galvanometer from damage due to heavy current.